

Arch: Single Cycle Processor

Alex Chi

Update: April 7, 2020

Contents

1	How to design a processor	1
1.1	Requirements of the Instruction	1
1.2	Components of the Data Path	1
1.3	Clocking Methodologies	2
1.4	Generic Steps of Datapath	2
2	Design	2
2.1	Fetch Instruction	2
2.2	Decoding Instruction	2
2.3	Data path for R-type	2
2.4	Decoding	3

1 How to design a processor

- Analyze instruction set (data path requirements) using RTL
 - refer to slides for examples
 - $\text{ADDU } R[rd] \leftarrow R[rs] + R[rt], PC \leftarrow PC + 4$

1.1 Requirements of the Instruction

- mem: inst & data
- registers: read rs, read rt, write rt or rd
- pc
- sign / zero extender
- ALU
- add 4

1.2 Components of the Data Path

- combinational elements
 - adder (A, B, CarryIn \rightarrow Sum, Carry)
 - MUX (A, B, Select \rightarrow Y)
 - ALU (A, B, Op \rightarrow result)
- storage elements
 - register file (RA, RB, RD, busW, WE, Clk \rightarrow busA, busB)
 - ideal memory (Address, WE, data in, Clk \rightarrow data out)

1.3 Clocking Methodologies

- state elements: register
- edge-triggered: all state changes occur on a clock edge
- cycle time = clk-to-Q + longest delay path + setup + clock skew

1.4 Generic Steps of Datapath

- Instruction Fetch
- Decode
- Execute
- Memory
- Register Write

2 Design

2.1 Fetch Instruction

- $PC = PC + 4$
- $Instruction = M[PC]$

2.2 Decoding Instruction

- rs: read addr 1
- rt: read addr 2
- rd: write addr
- use MUX to wire rt to write addr (lw, sw)

2.3 Data path for R-type

- add: $R[rd] = R[rs] \text{ op } R[rt]$
- ori: $R[rt] = R[rs] \text{ op } \text{imm (zero extended)}$
- lw: $Addr = R[rs] + \text{signext(imm)}, R[rt] = M[Addr]$
- sw: $Addr = R[rs] + \text{signext(imm)}, M[Addr] = R[rt]$
- beq: $PC = PC + 4 + \text{offset if } rs = rt \text{ else } PC + 4$
- try to draw the graph by yourself!

2.4 Decoding

- ALU
 - op code 2:0 for ALUop
 - func 3:0 for sub-op
 - just recite the table by induction: what operation should ALU do?
- Main Logic
 - use a lot of and gate to identify op
 - assemble main control (PLA)